

Midterm Check List

- 7400 series chips have 14 pins, pin#7=gnd and pin#14=Vcc
 - 74LS00 is NAND GATE
 - 74LS04 is NOT GATE
 - 74LS08 is AND GATE
 - 74LS32 is OR GATE
- Name of my TA is **Arzhang** and **Yuhan**
- Name of the FPGA chip used is **5CSEMA5F31C6**
- The depletion region in a pn junction causes which of the following?
 - Electric Field**
 - Hole electron recombination
 - semiconductor doping
 - current equilibrium**

Notice that the second option is a confusion option in this question. It is what happens/causes the depletion layer, but is not something that the depletion layer caused!
- More gates are needed to implement a positive edge triggered FF than are needed to implement a negedge FF.
 - True
 - False**

This question makes no sense... Completely unrelated questions!
- Remember the syntax of Verilog

```
module alu (Y, A, B, Select);
    input [3:0] A, B;
    input [1:0] Select;
    output reg[3:0] Y;
    always @(*)
        begin
            case (select)
                2'b00: Y = A & B; // Bitwise and
                2'b01: Y = A | B; // Bitwise or
                2'b10: Y = A ^ B; // Bitwise xor
                2'b11: Y = ~A; // Bitwise negate
                default: Y = 4'b1111; // Default fall back
            endcase
        end
endmodule
```

1. **Don't forget the default case, and note the begin and end statements following the always: declare the always scope.**
 2. **Remember to use non-blocking assignments for sequential circuits and the regular one for combinational circ**
7. The **maxterm** always looks like a sum (product of maxterm is when we combine multiple) and a **minterm** always looks like a product! Notice also that to qualify for a min/max term, it has to contain all the inputs (at least once?)
8. The most negative signed 8 bit number is **8'b10000000** which has decimal value of **-128**. Notice that **8'b10000000** \rightarrow **8'b01111111** \rightarrow **8'b10000000** which means negative of 2^7 so the result is **-128**. The most positive signed 8-bit binary number is **8'b01111111** which has value $2^7 - 1 = 127$. So we have 127 positive number, 128 negative numbers and we have zero!
9. The application of a voltage that causes junction current to stop flowing is called **reverse bias**
- In considering whether a bias on pn junction enlarges or shrinks the depletion layer, first consider the electrons!
- Forward bias means positive on positive. In this case, the depletion layer is weakened
 - Reverse bias means the opposite, and in this case the depletion layer grows thicker.
10. The charge carriers in a p-type material is called holes. **NOT BORON**. The charge carrier in the n-type material is electrons, there is nothing interesting here.
11. The K-map starts with the first slot in the first row corresponding to the **index 0**. Notice that K-Maps have oddity when it comes to the number three! Be carefull.
12. A FSM is said to have safe state transitions if all state transitions don't create glitch. E.g. a machine with states 01, 00, 11. If I make a transition from 00 to 11, it is possible that 00 first transits into 01 and then 11 which may cause unstable/odd behavior, this is not good. **Notice that no two states can have the same name!** Since if this ever happens, you won't be able to tell which state the machine is at and this could be hazzardous.
13. If you want a wire to be included in the Teck View in Quartusm what Verilog syntax term do you need to use: **/* Synthesis Keep */**
14. For a clocked SR latch, what are the outputs on Q and \bar{Q} when C, R, S are all high? **Q:1; Qbar:1** TRACE THIS!!
15. The four items in the lab box are
1. Wire Stripper
 2. Ribbon Cable
 3. Logic Probe
 4. Chip Puller
16. In a pn junction, any current/electron movement caused by a electric field is **drift** not diffusion.

17. JK flip flop

1. **JK = 11 Flips**
2. JK = 01 Kills, sets zero
3. JK = 10 Sets, sets one
4. JK = 00 holds

18. Consider a 6 to 1 mux. The complete truth table would require **512** rows. This is because since we have 3 bits for selection, and for each case, we have to enumerate all the possible input combinations of the 6 inputs (each assumed to be 1 bit wide). The total is then 2 to the power of 6 + 3.

19. The following error message is caused by **combinational @(*) block with missing cases in case block or missing else in if-else.**

```
Warning (10240): Verilog HDL Always Construct warning at mux.v(..):  
inferring latch(es) for variable .., which holds its previous value  
in one or more paths through the always construct...
```

20. In creating a comparator, remember to use the already computed eq result to help determine greater/less than etc.

21. A machine that has output dependent on both the prev state and the current input is **mealy machine** while a machine that outputs solely the state is a **moore machine**

22.